

Physics

Name _____

Date _____ Period ____ # _____

Ingrum 12/97

Topic 21 Review Worksheet

1. For Questions 1-10, write the letter of the correct answer to the left of the question.

- _____ 1. As resistors are added to a circuit in series, the current in the circuit.
(a) increases (b) decreases (c) remains the same
- _____ 2. As you plug in more appliances in your house, the total current in the circuit
(a) increases (b) decreases (c) remains the same
- _____ 3. As you plug in more appliances in your house, the total resistance
(a) increases (b) decreases (c) remains the same
- _____ 4. An ammeter connected in parallel with a battery and resistor will
(a) give the current in the circuit (b) read zero (c) measure the resistance of the battery (d) burn out
- _____ 5. A voltmeter has an internal resistance that is
(a) high (b) low
- _____ 6. An ammeter has an internal resistance that is
(a) high (b) low
- _____ 7. Current is the same throughout in a
(a) series circuit (b) parallel circuit
- _____ 8. The sum of the resistors is less than the smallest resistor in a
(a) series circuit (b) parallel circuit
- _____ 9. If you have three identical resistors in parallel and one is removed, the current through the remaining resistors
(a) increases (b) decreases (c) remains the same
- _____ 10. If one resistor in a parallel circuit is removed, the total current
(a) increases (b) decreases (c) remains the same

2. A 10 Ω resistor, a 20 Ω resistor, and a 30 Ω resistor are connected in series with a 120 V source. What is the current in the circuit?

2. _____

3. A 10.0 Ω resistor, a 20.0 Ω resistor, and a 30.0 Ω resistor are connected in parallel across a potential difference of 120 V. What is the current through the 20.0 ohm resistor?

3. _____


4. A 15.0 ohm resistor is connected in series with two 10.0 ohm resistors in parallel and a 120 V generator. What is the voltage drop across the 15.0 ohm resistor?

4. _____

5. The following appliances are all connected in parallel in one of the lines in the electrical system of a house: a 15 ohm electric fry pan, a 25 ohm refrigerator, a 20.0 ohm heater, and a 12 ohm toaster. The fuse in this line melts at 28 A. Will this arrangement of appliances cause the fuse to melt? Explain.

5. _____

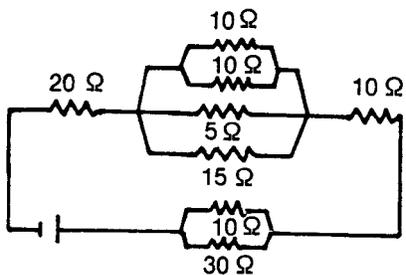6. Find the effective resistance of the circuit in the diagram.



6. _____

7. A 6 ohm resistor, a 54 ohm resistor, and a 32 ohm resistor are connected in series. Calculate their total resistance.

7. _____

8. Calculate the total resistance of four $8\ \Omega$ resistors connected in parallel.

8. _____

9. Two $12\ \Omega$ resistors and a $6\ \Omega$ resistor are each connected in parallel. A $15\ \Omega$ resistor is added to the parallel group in series. Calculate the voltage needed to drive a $2.0\ \text{A}$ current through the total resistance.

9. _____


10. Three resistors are connected in parallel across $20.0\ \text{V}$. The resistors draw a total of $5.0\ \text{A}$. Two of the resistors have values of $24\ \Omega$ and $12\ \Omega$. What is the value of the third resistor?

10. _____

11. A coffee pot rated at $360\ \text{W}$, an iron rated at $960\ \text{W}$, and an oven rated at $1200\ \text{W}$ are connected in parallel across $120\ \text{V}$. The $15\ \text{A}$ fuse in the circuit immediately blows. Calculate the total current drawn.


11. _____

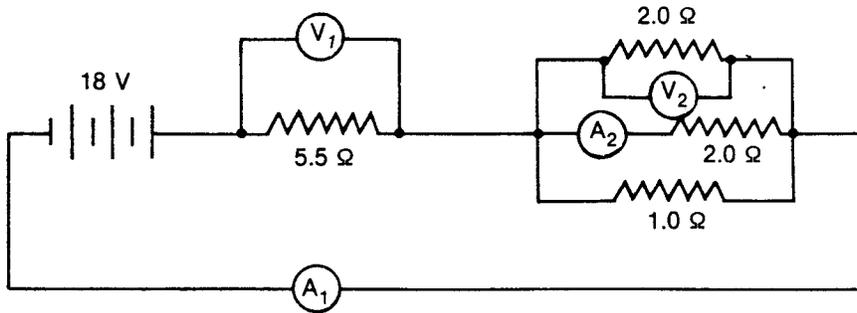12. Calculate the total resistance of the circuit shown below.



12. _____

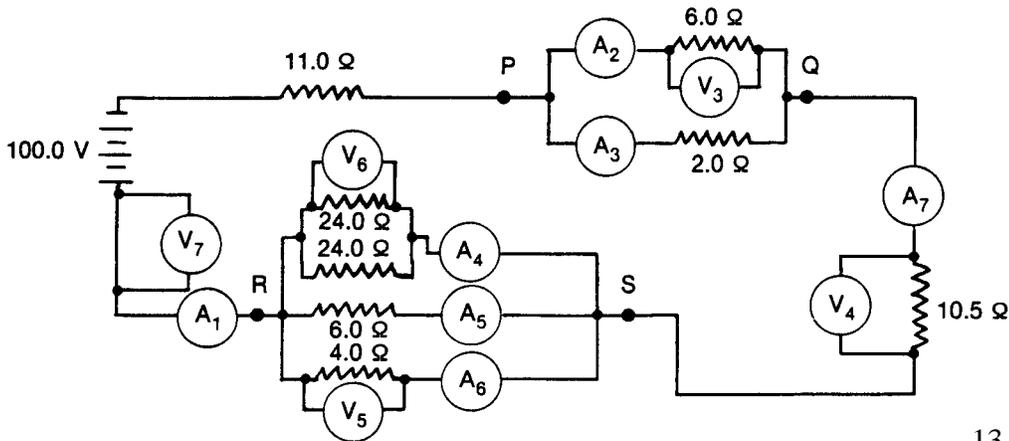13. What are the meter readings for the diagram in problem 12?



13. _____

14. Calculate the reading for each of the 7 ammeters in the circuit diagram below.

14. _____

15. Calculate the reading for each of the 5 voltmeters in the circuit diagram in problem 14.

15. _____