

Physics

Name _____

Date _____ Period # _____

Ingrum 12/97

Topic 21 Review Worksheet

1. For Questions 1-10, write the letter of the correct answer to the left of the question.

- b 1. As resistors are added to a circuit in series, the current in the circuit.
(a) increases (b) decreases (c) remains the same
- a 2. As you plug in more appliances in your house, the total current in the circuit
(a) increases (b) decreases (c) remains the same
- b 3. As you plug in more appliances in your house, the total resistance
(a) increases (b) decreases (c) remains the same
- d 4. An ammeter connected in parallel with a battery and resistor will
(a) give the current in the circuit (b) read zero (c) measure the resistance of the battery (d) burn out
- a 5. A voltmeter has an internal resistance that is
(a) high (b) low
- b 6. An ammeter has an internal resistance that is
(a) high (b) low
- a 7. Current is the same throughout in a
(a) series circuit (b) parallel circuit
- b 8. The sum of the resistors is less than the smallest resistor in a
(a) series circuit (b) parallel circuit
- c 9. If you have three identical resistors in parallel and one is removed, the current through the remaining resistors
(a) increases (b) decreases (c) remains the same
- b 10. If one resistor in a parallel circuit is removed, the total current
(a) increases (b) decreases (c) remains the same

2. A $10\ \Omega$ resistor, a $20\ \Omega$ resistor, and a $30\ \Omega$ resistor are connected in series with a $120\ \text{V}$ source. What is the current in the circuit?

$$R_T = 10 + 20 + 30 = 60\ \Omega$$

$$I = \frac{V}{R} = \frac{120\ \text{V}}{60\ \Omega}$$

2. 2A


3. A $10.0\ \Omega$ resistor, a $20.0\ \Omega$ resistor, and a $30.0\ \Omega$ resistor are connected in parallel across a potential difference of $120\ \text{V}$. What is the current through the $20.0\ \text{ohm}$ resistor?

$$\frac{1}{R_T} = \frac{1}{10} + \frac{1}{20} + \frac{1}{30} = \frac{6 + 3 + 2}{60}$$

$$I = \frac{V}{R} = \frac{120}{20} = 6$$

3. 6A

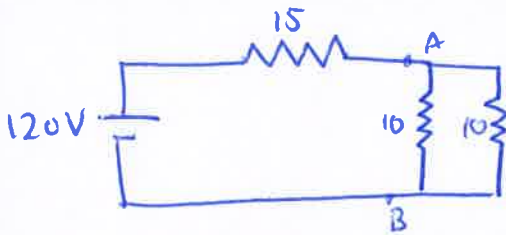4. A 15.0Ω resistor is connected in series with two 10.0Ω resistors in parallel and a 120 V generator. What is the voltage drop across the 15.0 ohm resistor?



$$\frac{1}{R_{AB}} = \frac{1}{10} + \frac{1}{10} = \frac{2}{10} = \frac{1}{5} \quad R_{AB} = 5$$

$$R_T = 15 + 5 = 20$$

$$I_T = \frac{120}{20} = 6 \text{ A}$$

$$V_{15} = 6 \times 15 = 90$$

4. 90V

5. The following appliances are all connected in parallel in one of the lines in the electrical system of a house: a 15Ω electric fry pan, a 25Ω refrigerator, a 20.0Ω heater, and a 12Ω toaster. The fuse in this line melts at 28 A . Will this arrangement of appliances cause the fuse to melt? Explain.


$$\frac{1}{R_T} = \frac{1}{15} + \frac{1}{25} + \frac{1}{20} + \frac{1}{12} =$$

$$R_T = 4.167 \Omega$$

$$I = \frac{120}{4.167} = 28.798$$

5. YES, Total current exceeds loading

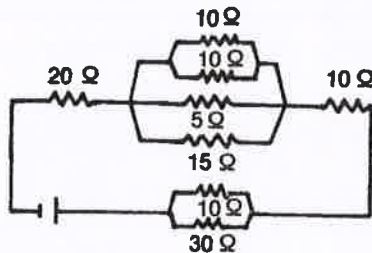6. Find the effective resistance of the circuit in the diagram.



$$20 + 2.143 + 10 + 7.5$$

6. 39.643 Ω


7. A 6Ω resistor, a 54Ω resistor, and a 32Ω resistor are connected in series. Calculate their total resistance.

7. 92 Ω

8. Calculate the total resistance of four $8\ \Omega$ resistors connected in parallel.

8. 2 Ω

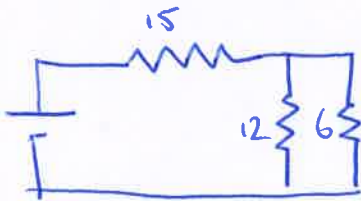9. Two $12\ \Omega$ resistors and a $6\ \Omega$ resistor are each connected in parallel. A $15\ \Omega$ resistor is added to the parallel group in series. Calculate the voltage needed to drive a $2.0\ \text{A}$ current through the total resistance.



$$R_T = 15 + 4$$


$$= 19\ \Omega$$

Since $I = 2$

$$V = 2 \times 19 = 38\text{V}$$

9. 38V

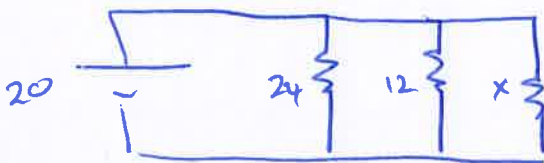10. Three resistors are connected in parallel across $20.0\ \text{V}$. The resistors draw a total of $5.0\ \text{A}$. Two of the resistors have values of $24\ \Omega$ and $12\ \Omega$. What is the value of the third resistor?



$$I_{24} = \frac{20}{24}$$

$$I_{12} = \frac{20}{12}$$

$$I_x = \frac{20}{x}$$

} 5

$$\frac{5}{6} + \frac{10}{6} + \frac{20}{x} = 5$$

$$\frac{15}{6} + \frac{20}{x} = 5$$

$$\frac{15x + 120}{6x} = 5$$

$$15x + 120 = 30x$$

$$120 = 15x$$

$$x = \frac{120}{15} = 8\ \Omega$$

10. 8 Ω

11. A coffee pot rated at $360\ \text{W}$, an iron rated at $960\ \text{W}$, and an oven rated at $1200\ \text{W}$ are connected in parallel across $120\ \text{V}$. The $15\ \text{A}$ fuse in the circuit immediately blows. Calculate the total current drawn.

Since $P = VI$ + $V = 120$

$$I_c = \frac{360}{120} = 3\ \text{A}$$


$$I_I = \frac{960}{120} = 8\ \text{A}$$

$$I_o = \frac{1200}{120} = 10\ \text{A}$$

$$I_T = 3 + 8 + 10 = 21\ \text{A}$$

11. 21A

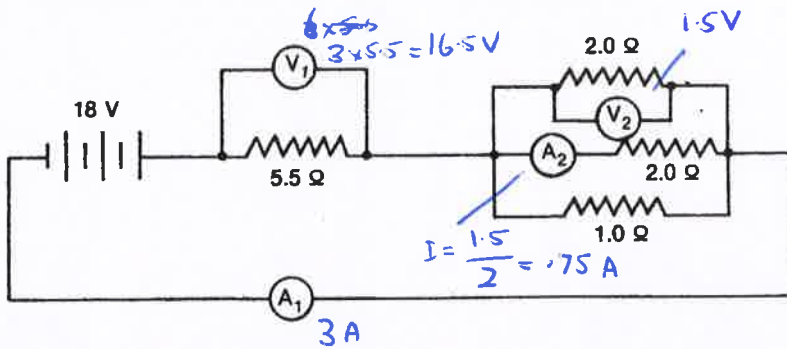12. Calculate the total resistance of the circuit shown below.



$$\frac{1}{R_1} = \frac{1}{2} + \frac{1}{1} + \frac{1}{2} = \frac{3}{2}$$


$$R_1 = \frac{2}{3}$$

$$R_T = 5.5 + 1.5$$

12. 6Ω

13. What are the meter readings for the diagram in problem 12?

$$I_T = \frac{18}{6} = 3A$$

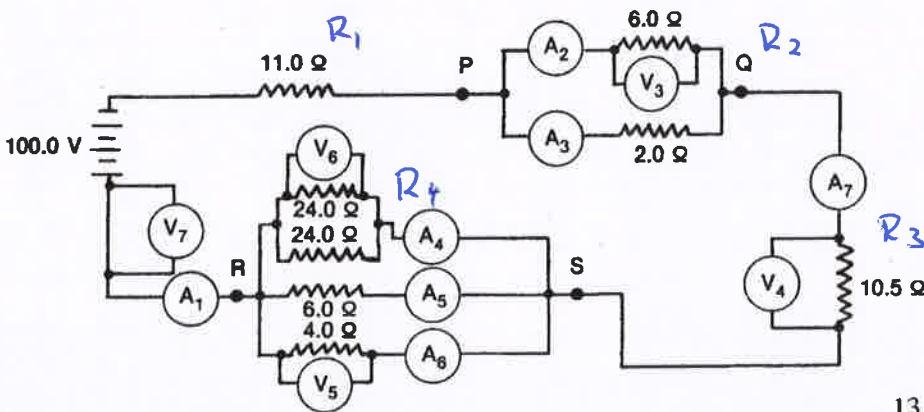

13. _____

14. Calculate the reading for each of the 7 ammeters in the circuit diagram below.

$$\frac{1}{R_2} = \frac{1}{6} + \frac{1}{2} = \frac{4}{6} \quad R_2 = \frac{3}{2} \Omega$$

$$\frac{1}{R_4} = \frac{1}{24} + \frac{1}{24} + \frac{1}{6} + \frac{1}{4} = \frac{1+1+4+6}{24} = \frac{12}{24} = \frac{1}{2} \quad R_4 = 2 \Omega$$

$$R_T = 11 + \frac{3}{2} + 10.5 + 2 = 25 \Omega$$

$$I_T = \frac{100}{25} = 4A$$

$$A_1 = 4A = A_7$$

$$A_2 = 1A$$

$$A_3 = 3A$$

$$A_4 = \frac{V_6}{12} = \frac{8}{12} = \frac{2}{3} A$$

$$A_5 = \frac{8}{6} = \frac{4}{3}$$

$$A_8 = \frac{8}{4} = 2A$$

$$\left. \begin{array}{l} A_4 = \frac{2}{3} A \\ A_5 = \frac{4}{3} \\ A_8 = 2A \end{array} \right\} = 4A$$

14. _____

15. Calculate the reading for each of the 5 voltmeters in the circuit diagram in problem 14.

$$V_{RS} = 4 \times 2 = 8V$$

$$= V_6 = V_5$$

$$V_4 = 4 \times 10.5 = 42V$$

$$V_7 = 0$$

$$V_3 = 1 \times 6 = 6V$$

15. _____