

Name: _____



Transformers

1. A neon sign requires 12,000 V for its operation. It operates from a 220 V supply.
 - a. What type of transformer is needed?
 - b. What must be the turns ratio, N_s/N_p of the transformer?
2. What happens to the output voltage when the number of turns on the secondary transformer coil is doubled?
3. A step-up transformer has 110 turns on its primary coil. Its secondary coil consists of 1455 turns. The primary coil received an AC current at 120 V.
 - a. What is the voltage across the secondary circuit?
 - b. The current in the secondary coil is 3.6 A. What current flows in the primary circuit?
 - c. What is the power input and output of the transformer?
4. The primary coil of a transformer has 700 turns and is connected to a 185 V source. How many turns would be needed in the secondary coil to supply 880 V?
5. In some places, insect zappers, with its blue lights, are a familiar sight on a summer's night. These devices use a high voltage to electrocute the insects. One such device uses an AC voltage of 4320 V, which is obtained from a standard 240 V outlet by means of a transformer. If the primary coil has 21 turns, how many turns are there in the secondary coil?
6. A generating station is producing 1.2×10^6 W of power that is to be sent to a small town that is 7 km away. Each of the two wires that comprise the transmission line has a resistance of 5.0×10^{-2} Ω /km.
 - a. Find the power lost in the heating of the wires if the power is transmitted at 1200 V.
 - b. A 100:1 step-up transformer is used to raise the voltage before the power is transmitted. How much power is now lost in heating the wires?

Answers

1a. step up b. 600/11 2. Doubled 3a. 1587 V b. 48A c. 5714 W 4. 3330 turns 5. 378 6a. 700,000W b 70 W